
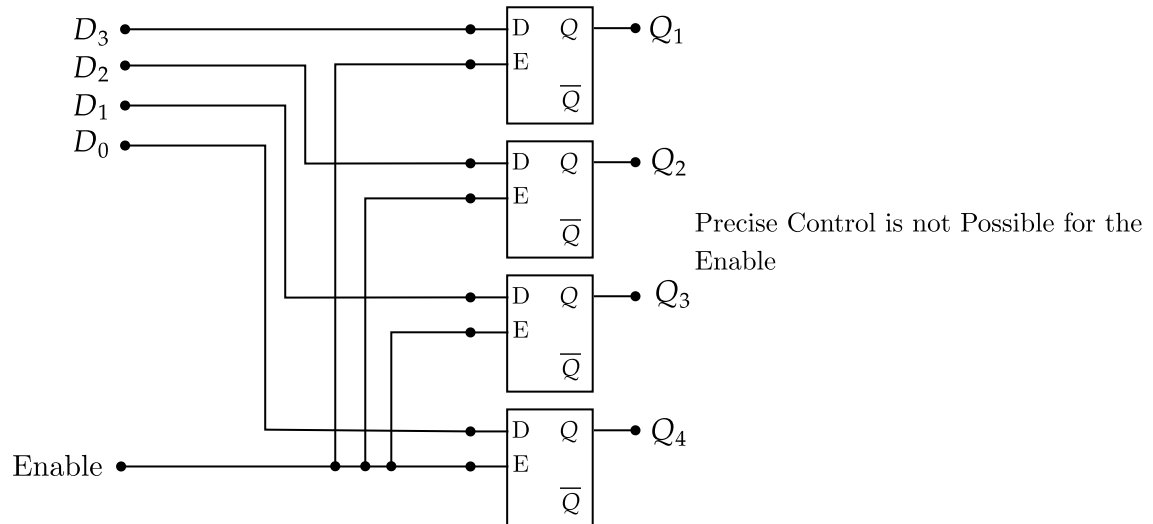


CONCEPT OF REGISTER

Register using D Latches

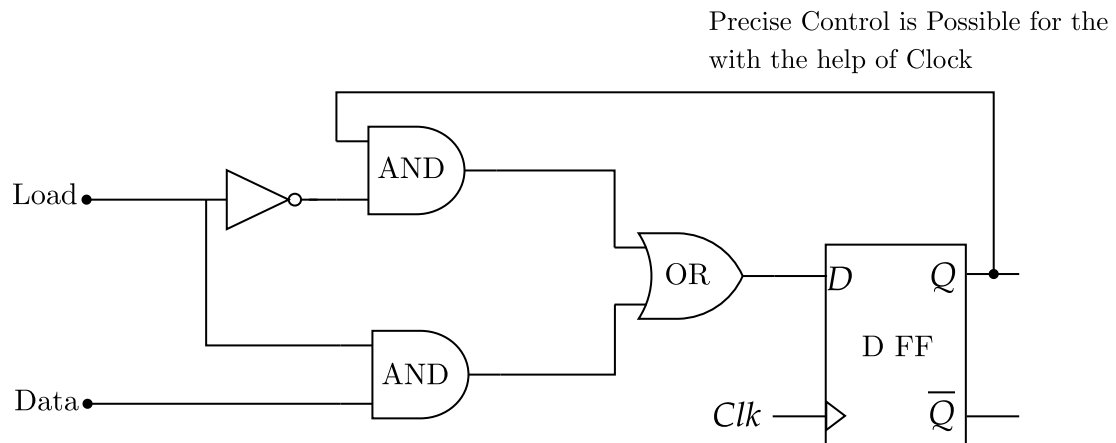


1 bit Register using D Flip Flop



Logic Diagram of Register

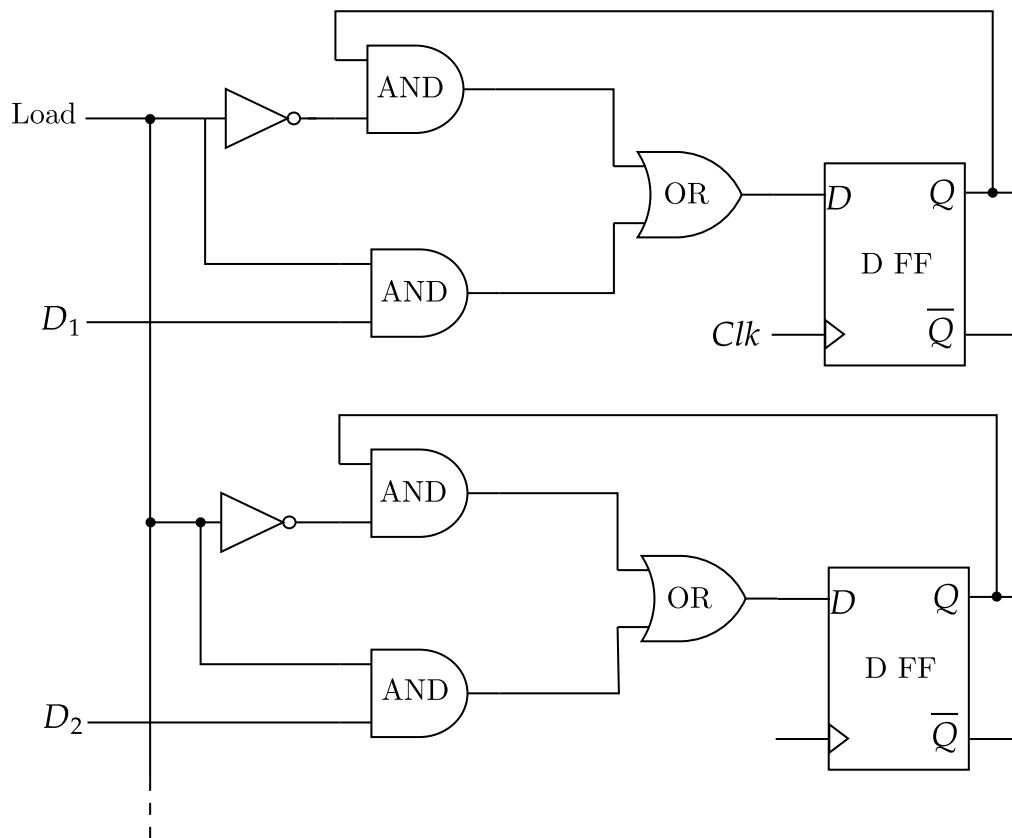Precise Control is Possible for the
Enable When Register designed using D FF



Circuit Diagram of 8 bit Register

