
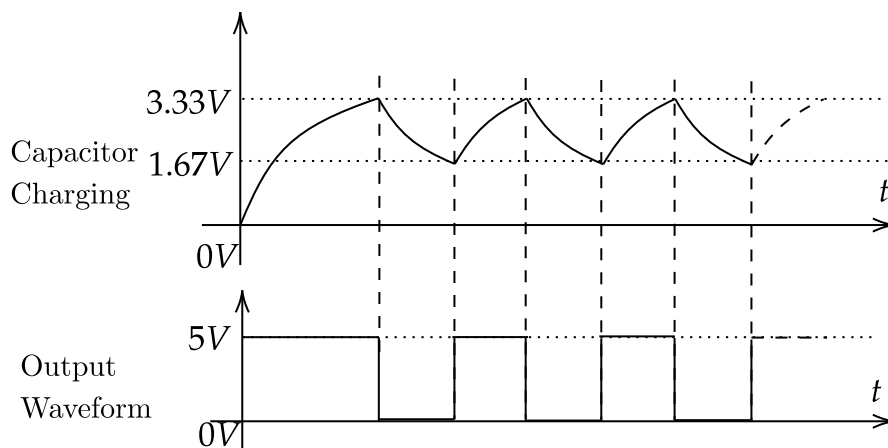


555 TIMER BASED 8 bit COMPUTER CLOCK CIRCUIT

Astable Circuit

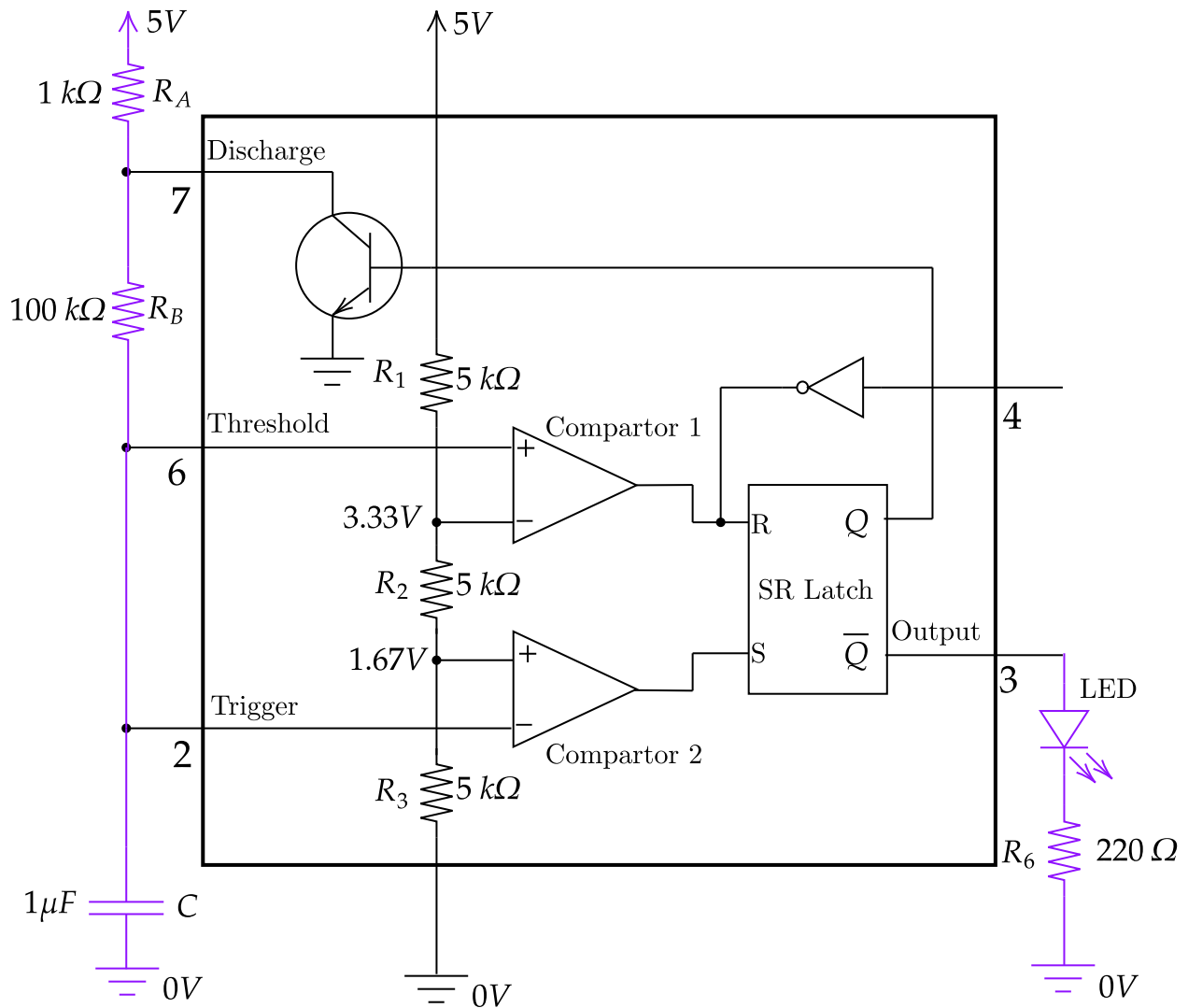



Charge Time

$$t_1 = 0.693(R_A + R_B) C$$


Discharge Time

$$t_2 = 0.693 R_B C$$

Monostable Circuit

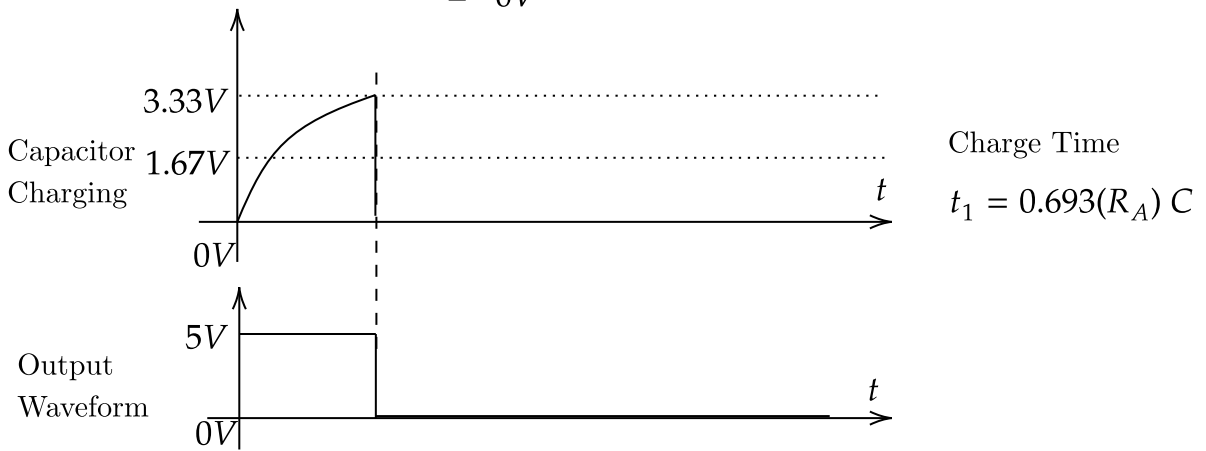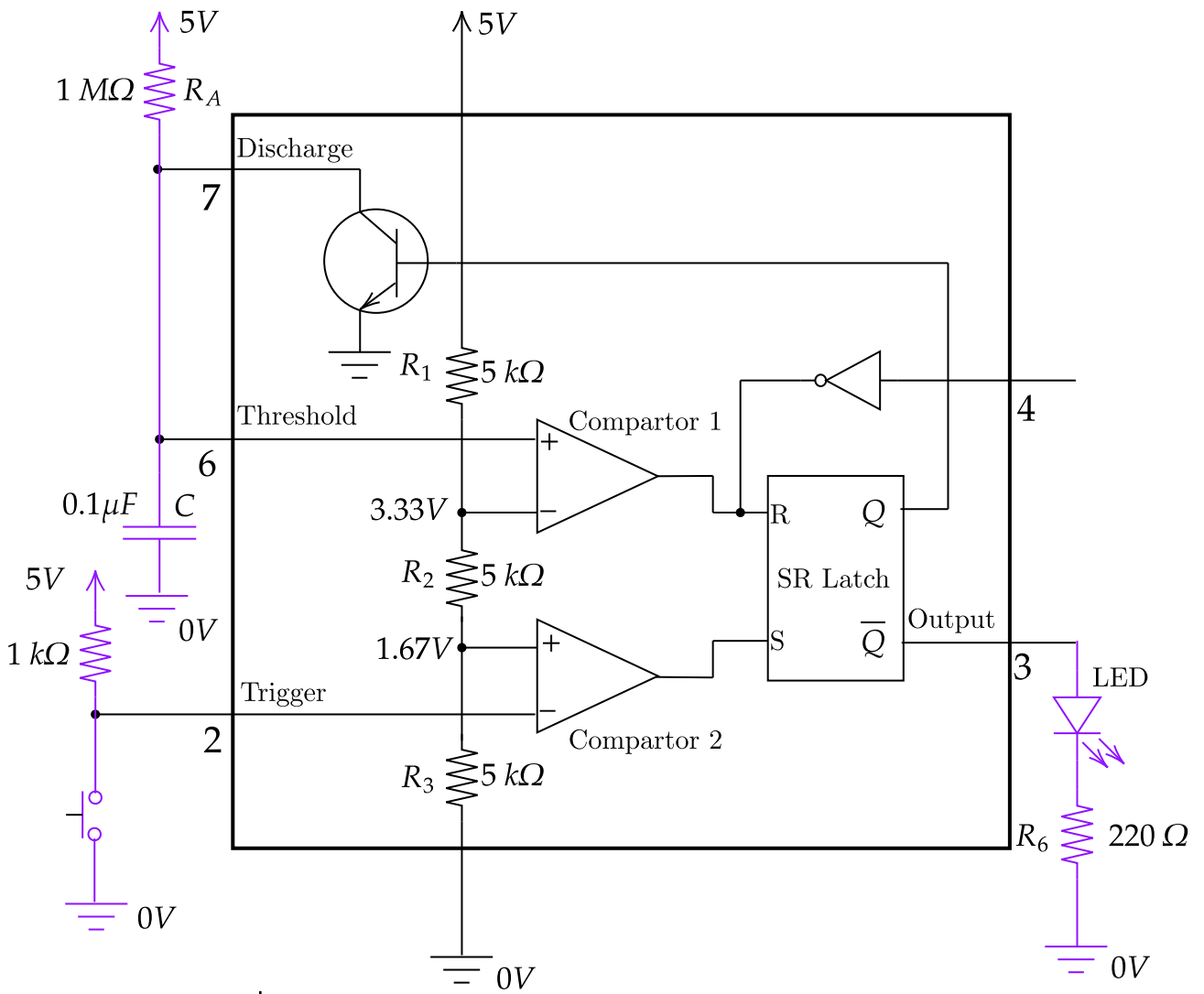

Bistable Circuit

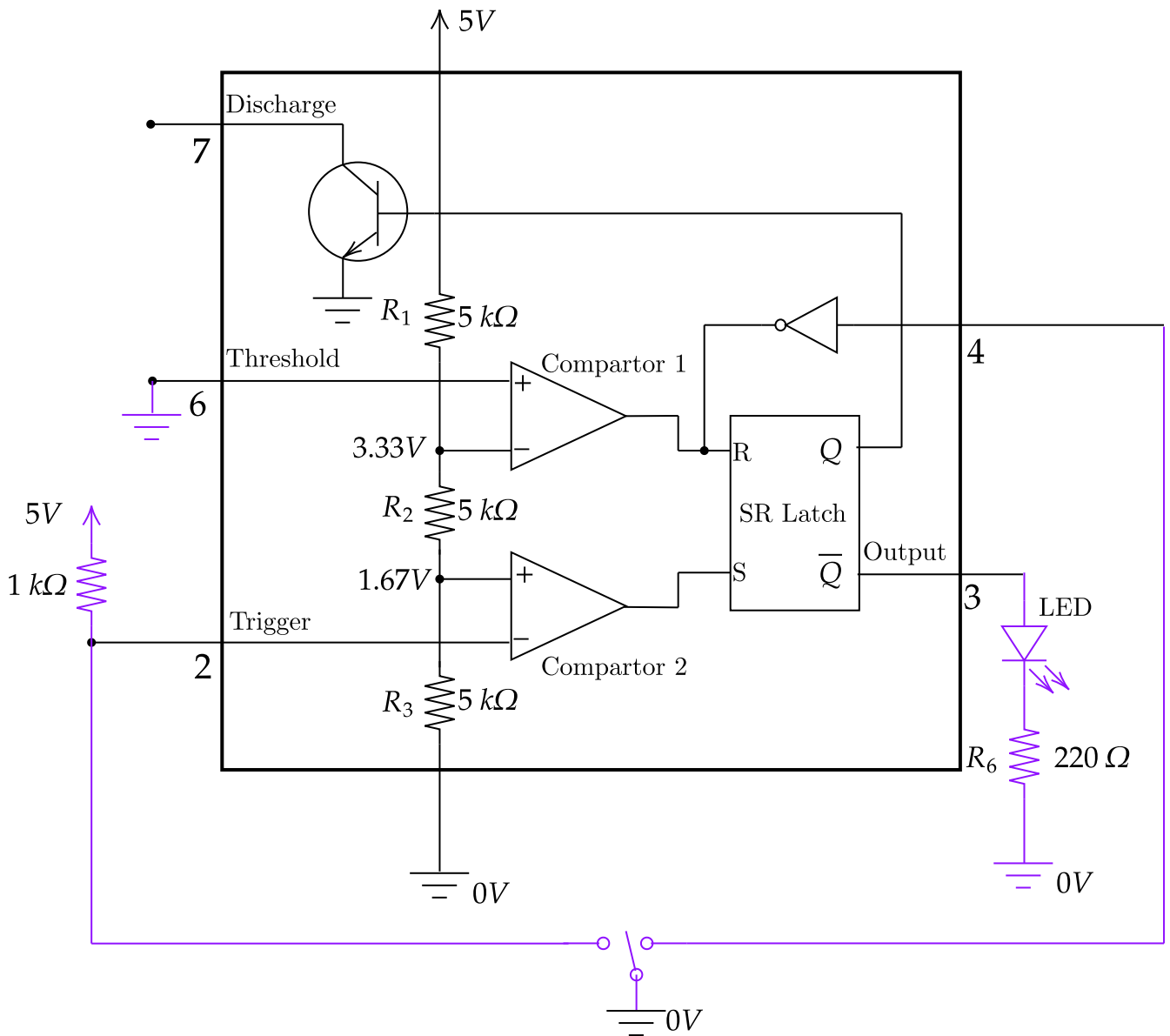

Clock Output Circuit

