
 


GATES USING TRANSISTORS


Buffer

 


Input	Output
High	High
Low	Low




Inverter

 


Input	Output
High	Low
Low	High

 


AND Gate

 


A	B	Out
Low	Low	Low
High	Low	Low
Low	High	Low
High	High	High

 


NAND Gate

 


A	B	Out
Low	Low	High
High	Low	High
Low	High	High
High	High	Low

 


OR Gate

 


A	B	Out
Low	Low	Low
High	Low	High
Low	High	High
High	High	High

 


NOR Gate

 


A	B	Out
Low	Low	High
High	Low	Low
Low	High	Low
High	High	Low

 

XOR Gate

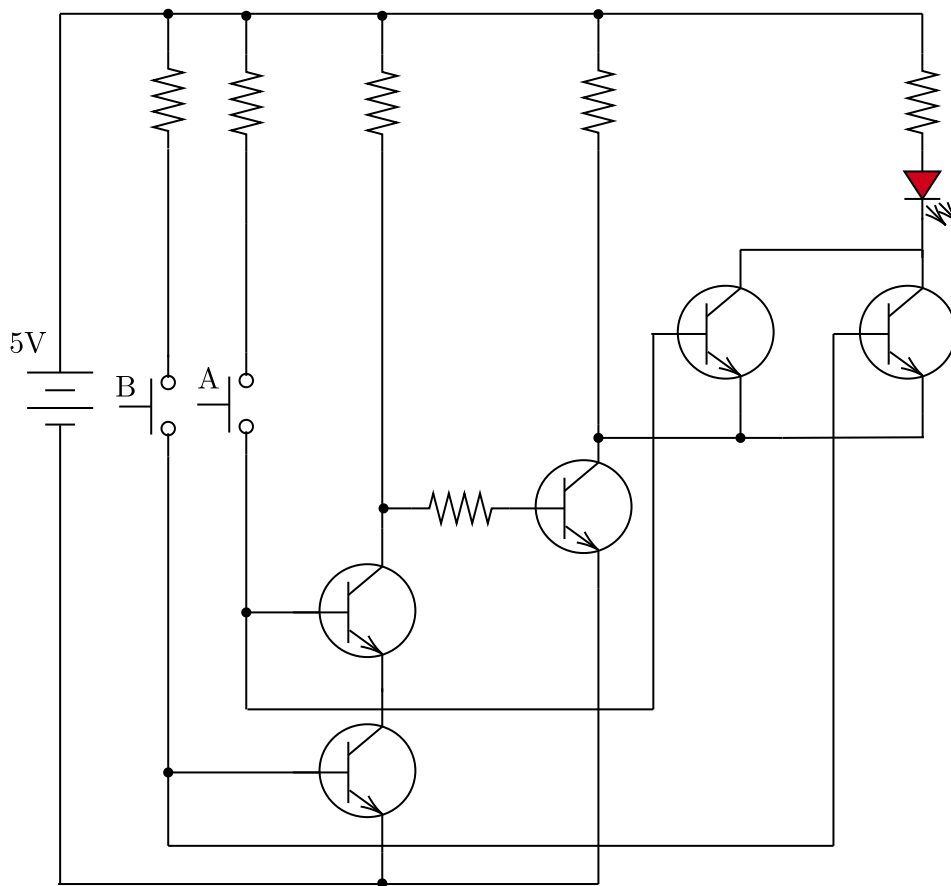

A	B	Out
Low	Low	Low
High	Low	High
Low	High	High
High	High	Low

 

XNOR Gate

